

CAD PROJECT VHDL

-- Libraries must import

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;
```

-- Create entity

```
entity EntityName is
    port ( InputPortName : in STD_LOGIC; -- STD_LOGIC used for 1 bit
          InputPortName: in STD_LOGIC_VECTOR (1 downto 0); -- STD_LOGIC_VECTOR(n downto 0) used for n bits
          OutputPortName: out STD_LOGIC_VECTOR (15 downto 0));
end EntityName;
```

-- Create architecture to manage behavior of our entity

```
architecture Behavioral of EntityName is
```

-- Create type for your entity

-- (for example for ram 256 address * 16 bit):

```
type TypeName is array(0 to 7) of STD_LOGIC_VECTOR (15 downto 0);
```

-- Create signal for your type/or for yourself to manage better process

```
signal SignalName: STD_LOGIC_VECTOR (15 downto 0) := x"0000";
```

```
begin
```

-- Create process

```
process (clk_in)
```

```
begin
```

```
    if rising_edge(clk_in) then
```

```
        case inputName is
```

```
            when "00" => SignalName <= x"0000";
```

```
            when "01" => SignalName <= STD_LOGIC_VECTOR(unsigned(SignalName) + 1);
```

```
            when others =>
```

```
        end case;
```


```
    end if;
```

```
end process;
```

```
    OutputName <= SignalName;
```

```
end Behavioral;
```

Test bench

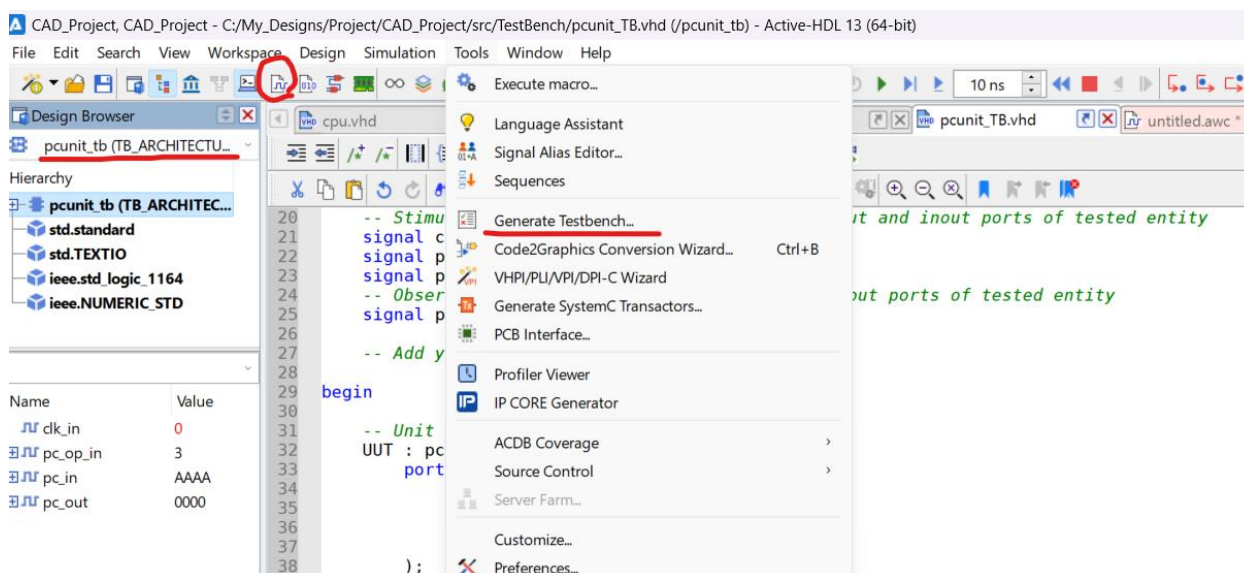

library ieee;

use ieee.NUMERIC_STD.all;

use ieee.std_logic_1164.all;

-- Add your library and packages declaration here ...

entity pcunit_tb is

end pcunit_tb;

architecture TB_ARCHITECTURE of pcunit_tb is

-- Component declaration of the tested unit

component pcunit

port(

clk_in : in STD_LOGIC;

pc_op_in : in STD_LOGIC_VECTOR(1 downto 0);

pc_in : in STD_LOGIC_VECTOR(15 downto 0);

pc_out : out STD_LOGIC_VECTOR(15 downto 0));

end component;

-- Stimulus signals - signals mapped to the input and inout ports of tested entity

signal clk_in : STD_LOGIC;

signal pc_op_in : STD_LOGIC_VECTOR(1 downto 0);

signal pc_in : STD_LOGIC_VECTOR(15 downto 0);

-- Observed signals - signals mapped to the output ports of tested entity

signal pc_out : STD_LOGIC_VECTOR(15 downto 0);

-- Add your code here ...

```
begin

    -- Unit Under Test port map

    UUT : pcunit

        port map (

            clk_in => clk_in,

            pc_op_in => pc_op_in,

            pc_in => pc_in,

            pc_out => pc_out

        );
```

-- Add your stimulus here ...

clk_process : process

```
begin

    clk_in <= '0';

    wait for 10 ns;

    clk_in <= '1';

    wait for 10 ns;

end process;
```

main_process: process

```
begin

    pc_op_in <= "00";

    pc_in <= (others => '0');

    wait for 100 ns;

    pc_op_in <= "01";

    wait for 20 ns;

    pc_op_in <= "10";

    pc_in <= x"AAAA";

    wait for 20 ns;

    pc_op_in <= "00";

    wait for 20 ns;

    pc_op_in <= "11";

    wait for 20 ns;
```

```
wait;

end process;

end TB_ARCHITECTURE;

configuration TESTBENCH_FOR_pcunit of pcunit_tb is

    for TB_ARCHITECTURE

        for UUT : pcunit

            use entity work.pcunit(behavioral);

        end for;


    end for;

end TESTBENCH_FOR_pcunit;
```

//

Pc Unit:

 when "00" => -- reset
when "01" => -- increment
when "10" => -- branch
when "11" => -- NOP



```
case pc_op_in is
    when "00" =>
        pc_out_signal <= x"0000";
    when "01" =>
        pc_out_signal <= STD_LOGIC_VECTOR(unsigned(pc_out_signal) + 1);
    when "10" =>
        pc_out_signal <= pc_in;
    when "11" =>
    when others =>
end case;
```

Control Unit:

when "000001" => -- Fetch

when "000010" => -- Decode

when "000100" => -- Reg read

when "001000" => -- Execute

when "010000" => -- Memory

when "100000" => -- Reg write



////////////////////////////////////

• Instruction	Form	Implementation	Condition bit	OPCODE
ST	URR	memory(rM) = rN	c: N/A	1101
LD	RRU	rD = memory(rM)	c: N/A	1100


////////////////////////////////////

```

case stage_out_signal is
  when "000001" =>
    stage_out_signal <= "000010";
  when "000010" =>
    stage_out_signal <= "000100";
  when "000100" =>
    stage_out_signal <= "001000";
  when "001000" =>
    if alu_op_in(3 downto 0) = "1100" or alu_op_in(3 downto 0) = "1101" then
      stage_out_signal <= "010000";
    else
      stage_out_signal <= "100000";
    end if;
  when "010000" =>
    stage_out_signal <= "100000";
  when "100000" =>
    stage_out_signal <= "000001";
  when others =>
    stage_out_signal <= "000001";
end case;

```


Decoder:

 

=====

• Instruction	Form	Implementation	Condition bit	OPCODE
ADD	RRR	$rD = rM + rN$	c: 1/0 = signed/unsigned	0000
SUB	RRR	$rD = rM - rN$	c: 1/0 = signed/unsigned	0001
NOT	RRU	$rD = \text{not } rN$	c: N/A	0010
AND	RRR	$rD = rM \text{ and } rN$	c: N/A	0011
OR	RRR	$rD = rM \text{ or } rN$	c: N/A	0100
XOR	RRR	$rD = rM \text{ xor } rN$	c: N/A	0101
LSL	RRI(5)	$rD = rM \ll rN$	c: N/A	0110
LSR	RRI(5)	$rD = rM \gg rN$	c: N/A	0111
CMP	RRR	$rD = \text{cmp}(rM, rN)$	c: 1/0 = signed/unsigned	1000
B	UI(8)	$PC = rM \text{ or } 8\text{-bit immediate}$	c: 1/0 = rM/8-bit immediate	1001
BEQ	URR	$PC = rM \text{ conditional on } rN$	c: N/A	1010
IMMEDIATE	RI(8)	$rD = 8\text{-bit immediate}$	c: 1/0 = upper/lower 8-bits	1011
LD	RRU	$rD = \text{memory}(rM)$	c: N/A	1100
ST	URR	$\text{memory}(rM) = rN$	c: N/A	1101

ALU:

 

1) Define signal (bothPositive,bothNegative,signedAdd,signedSub,overflow)

```
architecture Behavioral of alu is
    signal bpositive_signal : STD_LOGIC;
    signal bnegative_signal : STD_LOGIC;
    signal signed_add_signal : STD_LOGIC_VECTOR (15 downto 0);
    signal signed_sub_signal : STD_LOGIC_VECTOR (15 downto 0);
    signal overflow_signal : STD_LOGIC;
begin
    process(clk_in)
    begin
        if rising_edge(clk_in) then
            if enable_in='1' then

                signed_add_signal <= STD_LOGIC_VECTOR(signed(rM_data_in) + signed(rN_data_in));
                signed_sub_signal <= STD_LOGIC_VECTOR(signed(rM_data_in) - signed(rN_data_in));
                rD_write_enable_out <= rD_write_enable_in;

                if rM_data_in(rM_data_in'left) = '0' and rN_data_in(rN_data_in'left) = '0' then
                    bpositive_signal <= '1';
                else
                    bpositive_signal <= '0';
                end if;

                if rM_data_in(rM_data_in'left) = '1' and rN_data_in(rN_data_in'left) = '1' then
                    bnegative_signal <= '1';
                else
                    bnegative_signal <= '0';
                end if;

                if (signed(signed_add_signal) < 0 and bpositive_signal = '1') or (signed(signed_sub_signal) > 0 and bnegative_signal = '1') then
                    overflow_signal <= '1';
                else
                    overflow_signal <= '0';
                end if;
            end if;
        end if;
    end process;
end architecture;
```

2) Define instructions based attention to signals

```
-- BEQ
when "1010" =>
    if rN_data_in(14) = '1' then
        result_out <= rM_data_in;
        branch_out <= '1';
    else
        branch_out <= '0';
    end if;

-- IMMEDIATE
when "1011" =>
    if alu_op_in(4) = '1' then
        result_out <= imm_data_in & x"00";
    else
        result_out <= x"00" & imm_data_in;
    end if;
    branch_out <= '0';

-- LD
when "1100" =>
    result_out <= rM_data_in;
    branch_out <= '0';

-- ST
when "1101" =>
    result_out <= rM_data_in;
    branch_out <= '0';

when others =>
    NULL;
```



```

case alu_op_in(3 downto 0) is
-- ADD
when "0000" =>
    if alu_op_in(4) = '1' then
        if overflow_signal = '1' then
            result_out <= signed_add_signal;
        else
            result_out <= signed_add_signal;
        end if;
    else
        result_out <= STD_LOGIC_VECTOR(unsigned(rM_data_in) + unsigned(rN_data_in));
    end if;
    branch_out <= '0';

-- SUB
when "0001" =>
    if alu_op_in(4) = '1' then
        if overflow_signal = '1' then
            result_out <= signed_sub_signal;
        else
            result_out <= signed_sub_signal;
        end if;
    else
        result_out <= STD_LOGIC_VECTOR(unsigned(rM_data_in) - unsigned(rN_data_in));
    end if;
    branch_out <= '0';

-- NOT
when "0010" =>
    result_out <= not rM_data_in;
    branch_out <= '0';

-- AND
when "0011" =>
    result_out <= rM_data_in and rN_data_in;
    branch_out <= '0';

-- OR
when "0100" =>
    result_out <= rM_data_in or rN_data_in;
    branch_out <= '0';

-- XOR
when "0101" =>
    result_out <= rM_data_in xor rN_data_in;
    branch_out <= '0';

-- LSR
when "0110" =>
    result_out <= STD_LOGIC_VECTOR(shift_left(unsigned(rM_data_in), to_integer(unsigned(rN_data_in(3 downto 0)))));
    branch_out <= '0';

-- LSL
when "0111" =>
    result_out <= STD_LOGIC_VECTOR(shift_right(unsigned(rM_data_in), to_integer(unsigned(rN_data_in(3 downto 0)))));
    branch_out <= '0';

-- CMP
when "1000" =>
    -- negative bit
    if alu_op_in(4) = '1' and signed(signed_sub_signal) < 0 then
        result_out(15) <= '1';
    else
        result_out(15) <= '0';
    end if;
    -- zero bit
    if unsigned(rM_data_in) - unsigned(rN_data_in) = 0 then
        result_out(14) <= '1';
    else
        result_out(14) <= '0';
    end if;
    -- carry bit
    if alu_op_in(4) = '0' and unsigned(rM_data_in) - unsigned(rN_data_in) > unsigned(rM_data_in) + unsigned(rN_data_in) then
        result_out(13) <= '1';
    else
        result_out(13) <= '0';
    end if;
    -- overflow bit
    if alu_op_in(4) = '1' and overflow_signal = '1' then
        result_out(12) <= '1';
    else
        result_out(12) <= '0';
    end if;

    result_out(11 downto 0) <= x"000";
    branch_out <= '0';

-- B
when "1001" =>
    if alu_op_in(4) = '1' then
        result_out <= x"00" & imm_data_in;
    else
        result_out <= rM_data_in;
    end if;
    branch_out <= '1';

```